

NARAYANA SCHOOL STUDENT PROUDLY PRESENTS

SAMSUNG CHIP DESIGN FOR HIGH SCHOOL

WEEK 6 LABS-"COFFEE MACHINE"

**Vikranth majeti
1-21-2025**

Let me explain the NOT gate part step by step. The NOT gate inverts the signal it receives as input. If the input is 1 (High), the output becomes 0 (Low), and vice versa.

In this project, we need NOT gates to handle specific conditions where we require the opposite state of the input.

Why We Need NOT Gates

1. Milk Temperature (T):

- If T is 1, the milk is cold, and we don't want to dispense coffee or milk.
- We need a signal that is 1 when T is 0 (milk is hot).
- Use a NOT gate to invert T so that:
 - Input: T = 1 (cold) → Output: NOT_T = 0.
 - Input: T = 0 (hot) → Output: NOT_T = 1.

2. Milk Availability (M):

- If M is 0, milk is unavailable, and we need to indicate insufficient quantity.
- Use a NOT gate to invert M so that:
 - Input: M = 1 (available) → Output: NOT_M = 0.
 - Input: M = 0 (unavailable) → Output: NOT_M = 1.

3. Coffee Powder Availability (C):

- If C is 0, coffee powder is unavailable, and we need to prevent dispensing coffee.
- Use a NOT gate to invert C so that:
 - Input: C = 1 (available) → Output: NOT_C = 0.
 - Input: C = 0 (unavailable) → Output: NOT_C = 1.

How to Add NOT Gates in Wokwi

1. Click the "+" (Add Parts) button in Wokwi.
 2. Search for NOT Gate.
 3. Place the NOT gates near the inputs you need to invert (T, M, and C).
 4. Connect the input of the NOT gate to the button (e.g., T for temperature).
 5. Use the output of the NOT gate (NOT_T, NOT_M, or NOT_C) in your logic circuit.
-

NOT Gate Connections

Here's how you connect the NOT gates:

1. Inverting T for Hot Milk:
 - Connect the T button to the input of the NOT gate.
 - Label the NOT gate's output as NOT_T (this is 1 when milk is hot).
 2. Inverting M for Insufficient Quantity:
 - Connect the M button to the input of the NOT gate.
 - Label the NOT gate's output as NOT_M (this is 1 when milk is unavailable).
 3. Inverting C for Coffee Powder:
 - Connect the C button to the input of the NOT gate.
 - Label the NOT gate's output as NOT_C (this is 1 when coffee powder is unavailable).
-

Example of NOT Gate in Wokwi

1. Add a button for T (temperature).
2. Add a NOT gate.
3. Connect the button's output to the NOT gate's input.
4. Use the NOT gate's output (NOT_T) in your circuit for coffee and milk dispensing logic.

